



Logic Gates

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- Basics of Logic Gates



Logic gate



- Building blocks of digital electronic circuits.
- Boolean functions are implemented in digital circuits using these **logic gates**.
- Most logic gates have 2 inputs and 1 output.
- At any time, every terminal will be in one of the two binary conditions LOW (FALSE; 0; 0V) or HIGH (TRUE; 1; +5V).
- The function of each logic gate will be represented by Boolean expression



Logic gate




- Logic gates are classified into:
 - Basic gates : OR, AND, NOT
 - Universal gate : NAND, NOR
 - Special purpose gates: EX-OR, EX-NOR
- Truth table explains all the outputs of a logic circuit for all possible inputs to that circuits.




AND gate

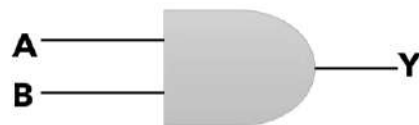- The realization of logical AND operator .
- Logic expression, **$Y = A.B$ or AB**
- The circuit will give high output (1) if both inputs are high otherwise, the output is low



Logic symbol

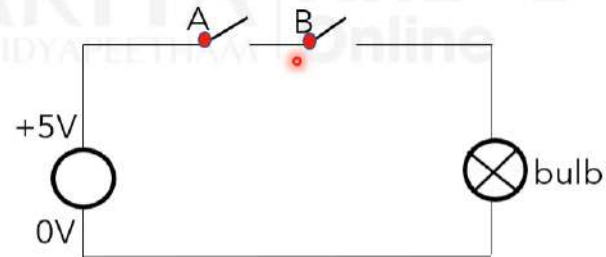

Switching circuit


inputs		output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Truth table

OR Gate



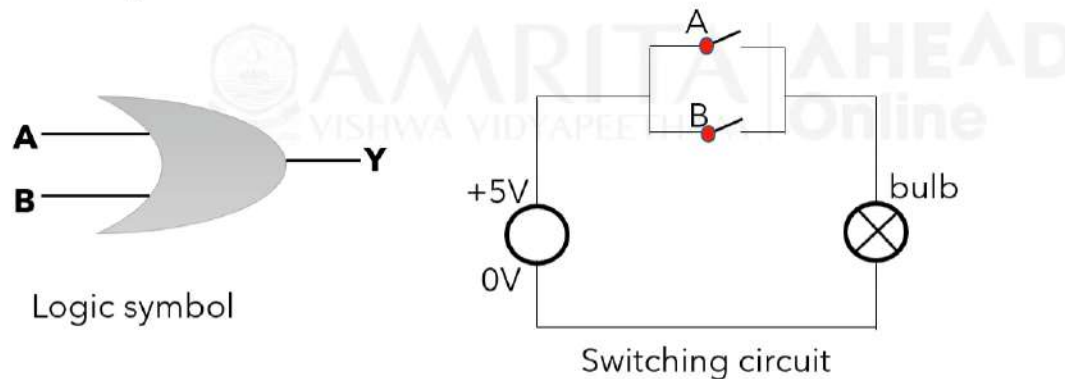- Logic expression, $Y=A+B$
- The circuit will give high output if any one input is high otherwise the output is low.





inputs		output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Truth table

NOT Gate



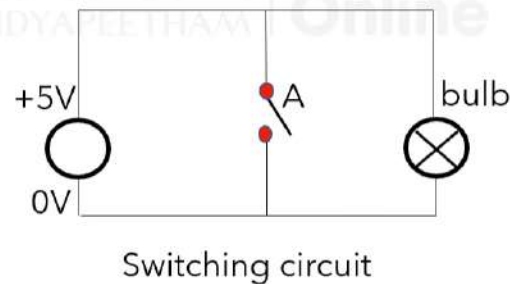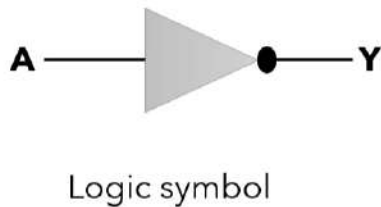- Single input single output gate.
- Also called Inverter because it inverts the given binary input.
- Logic expression, $Y = A' = \bar{A}$



input	output
A	Y
0	1
1	0

Truth table

NAND Gate



- NAND is a combination of AND gate and NOT gate
NOT + AND = NAND

- The circuit will give high (1) output if any one input is low (0) otherwise, the output is low (0).

- Logical expression, $Y = \overline{A.B}$



inputs		output
A	B	$Y = \overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

NOR Gate




- NOR is a combination of OR gate and NOT gate.

$$\text{NOT} + \text{OR} = \text{NOR}$$

- The circuit will give high (1) output if both inputs is low (0) otherwise the output is high (1).

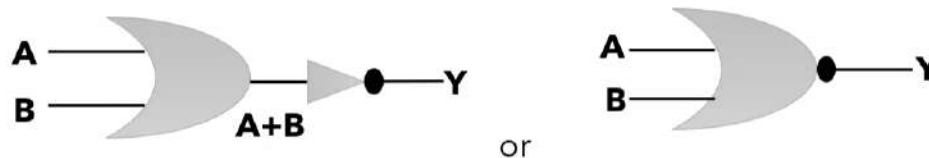- Logical expression, $Y = \overline{A+B}$




inputs		output
A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Truth table

XOR Gate



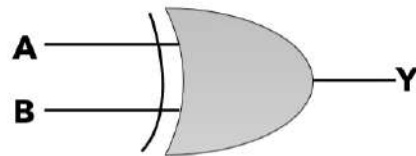- Exclusive-OR gate
- The output is high if the circuit input has odd number of 1's otherwise the output is low i.e., with even number of 1's.
- Logical expression **$Y = A \oplus B = A'B + AB'$** (SOP)



inputs		output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Truth table

X-NOR Gate



- Exclusive NOR gate or equivalence.
- The output is high if the circuit input has even number of 1's otherwise the output is low.
- Logical expression **$Y = A \odot B = A'B' + AB$**

Complement of XOR

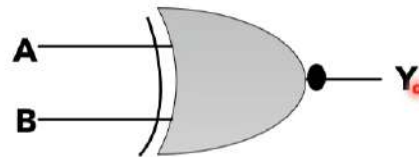

inputs		output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Truth table

Realizing Logic circuit from function



- Boolean Function, **$F = x + y'z$**


input variable : x, y, z

- Truth table

3 input variables = 2^3 combinations

- Logic circuit

literals - 3 (x, y', z) and 2 terms


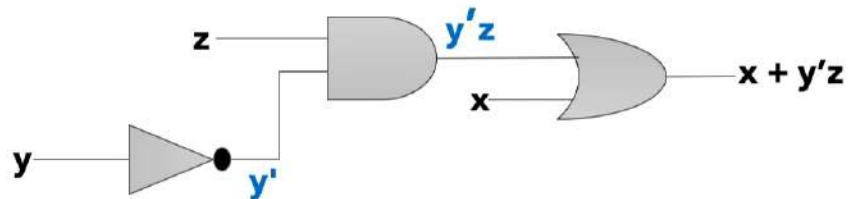


inputs			output
x	y	z	$F = x + y'z$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

→ $x = 0, y = 1, z = 0$
 $F = 0 + 1'.0$
 $= 0 + 0.0$
 $= 0 + 0$
 $= 0$

→ $x = 1, y = 1, z = 0$
 $F = 1 + 1'.0$
 $= 1 + 0.0$
 $= 1 + 0$
 $= 1$

Realizing function from Logic circuit

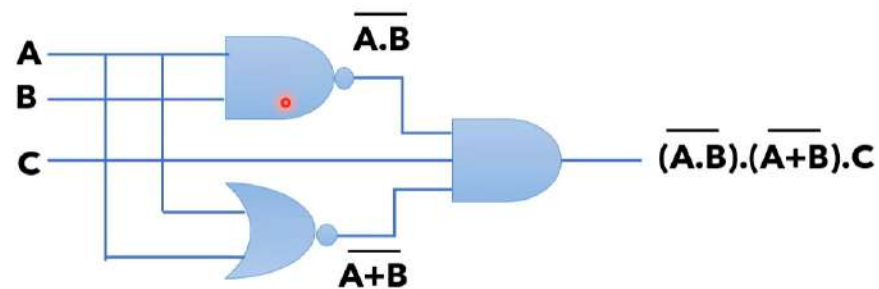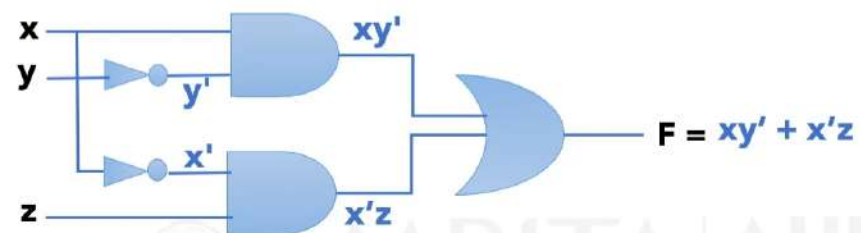

Summary

- Basics of Logic gates





Universal Logic Gate

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective


- Universal Logic gates
 - NAND gate
 - NOR gate




Introduction

- **NAND & NOR** gate are known as the **universal gates**.
- These gates alone sufficient to implement any Boolean expression and are inexpensive.
- Basic logic gates (AND, OR and NOT) are logically complete.
- Sufficient to show that AND, OR and NOT can be implemented with NAND and NOR gate.


Universal NAND gate

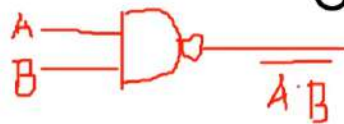

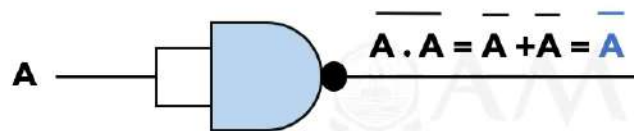
- We can implement NOT, AND and OR gates by combining one or more NAND gates.



(a) NOT gate implementation

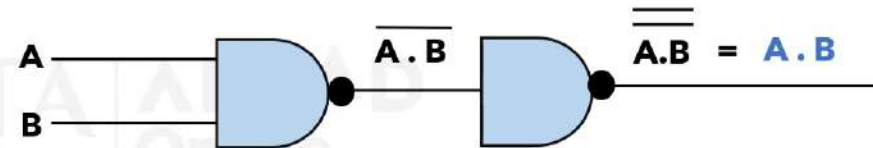


(b) AND gate implementation

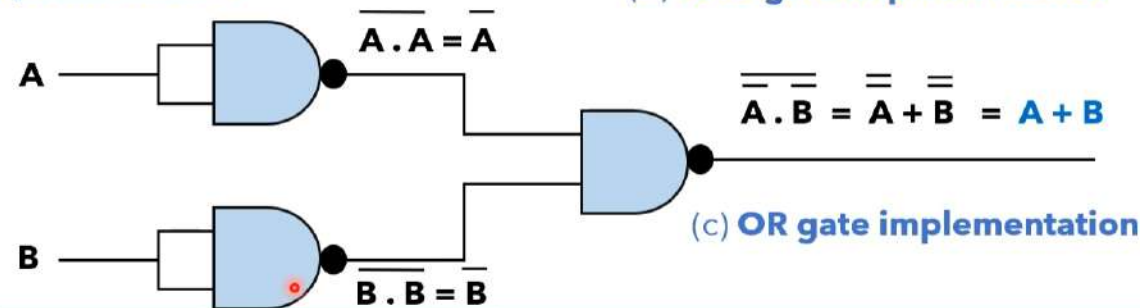


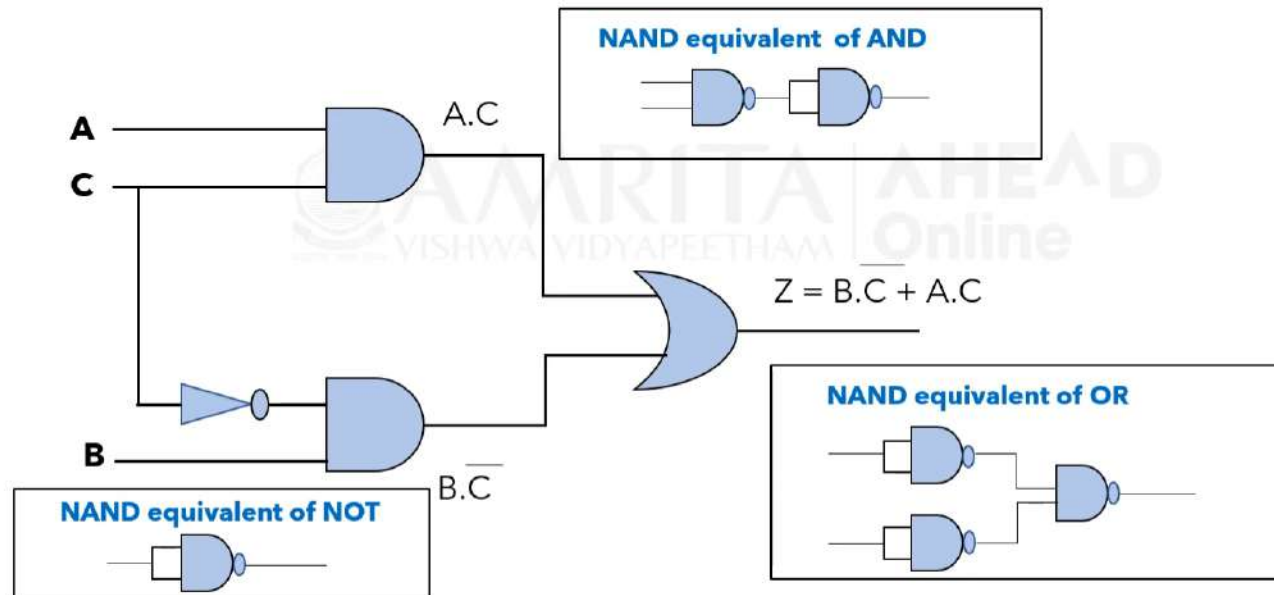
(c) OR gate implementation

NAND Logic circuit


- Design NAND logic circuit for the Boolean expression $Z = \overline{B.C} + A.C$




NAND logic circuit

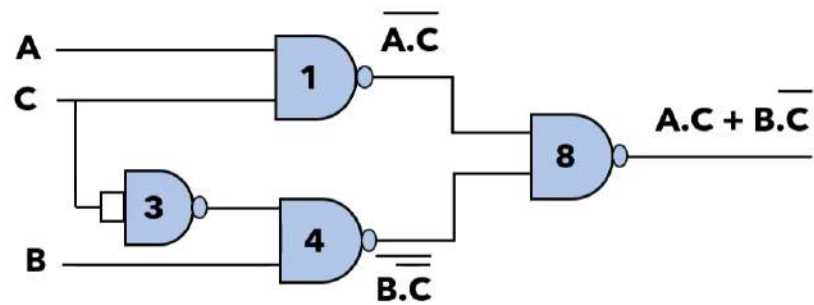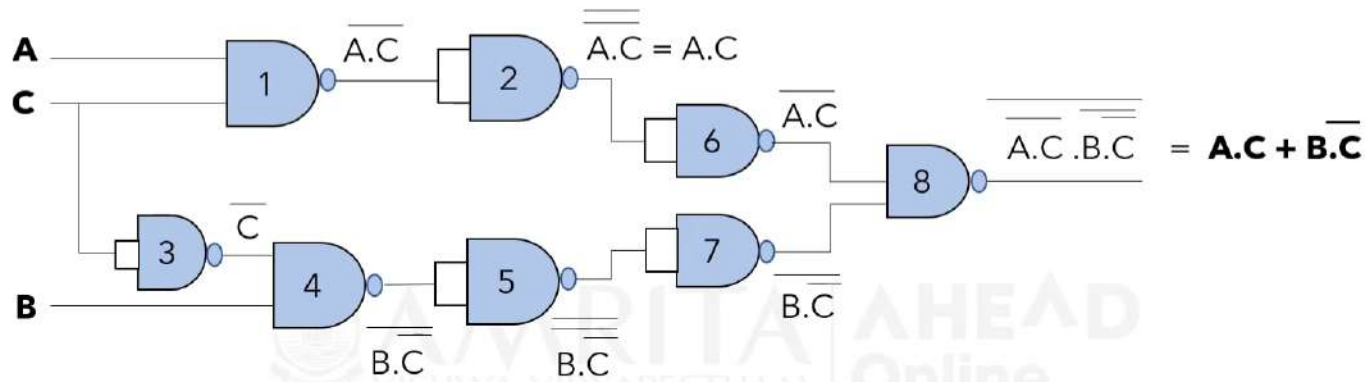


Universal NOR gate

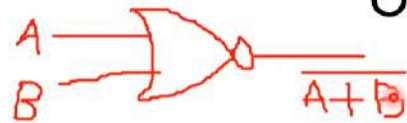

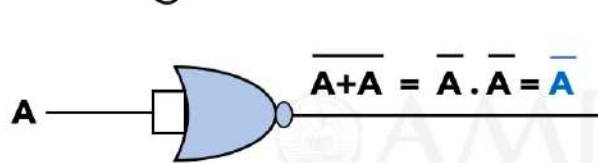
- Implement NOT, AND and OR gates by combining one or more NOR gates.



(a) **NOT gate implementation**

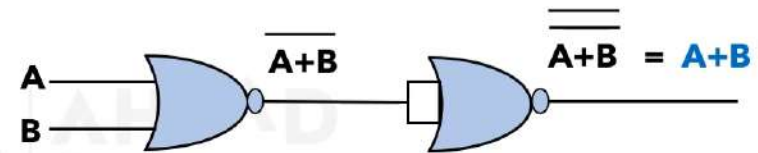


(b) **OR gate implementation**

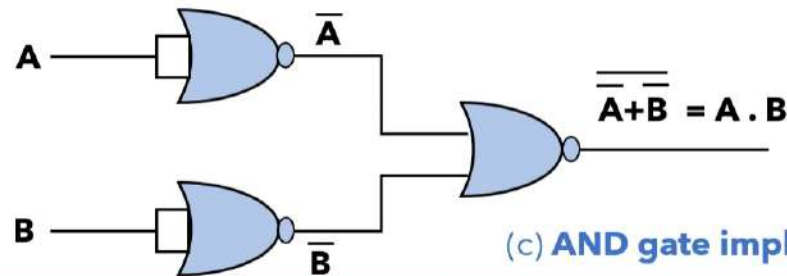

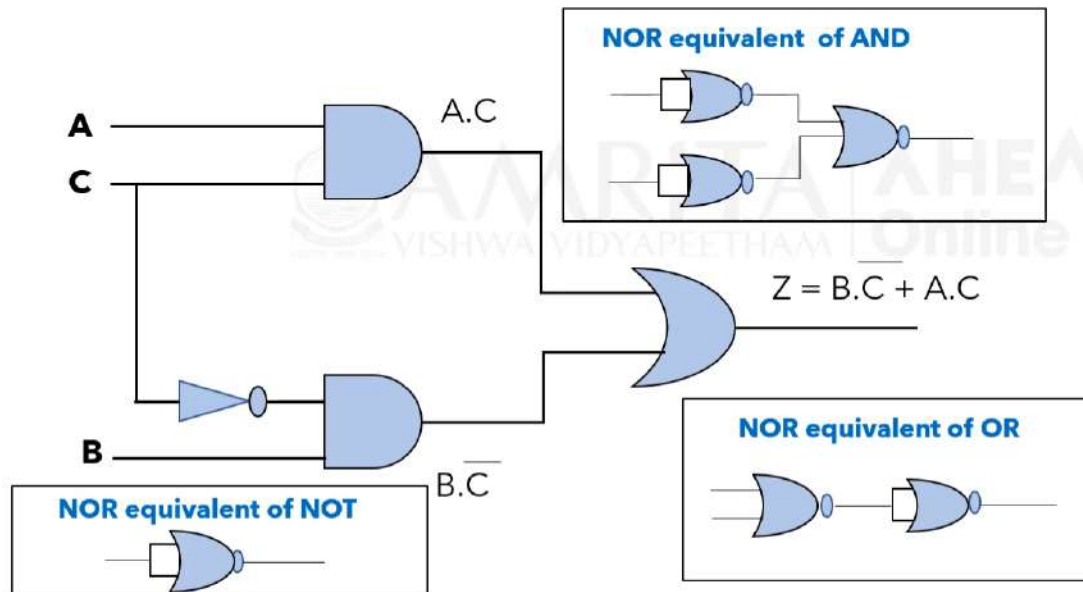
(c) **AND gate implementation**

NOR Logic circuit

- Design NOR logic circuit for the Boolean expression $Z = \overline{B.C} + A.C$



NOR Logic circuit

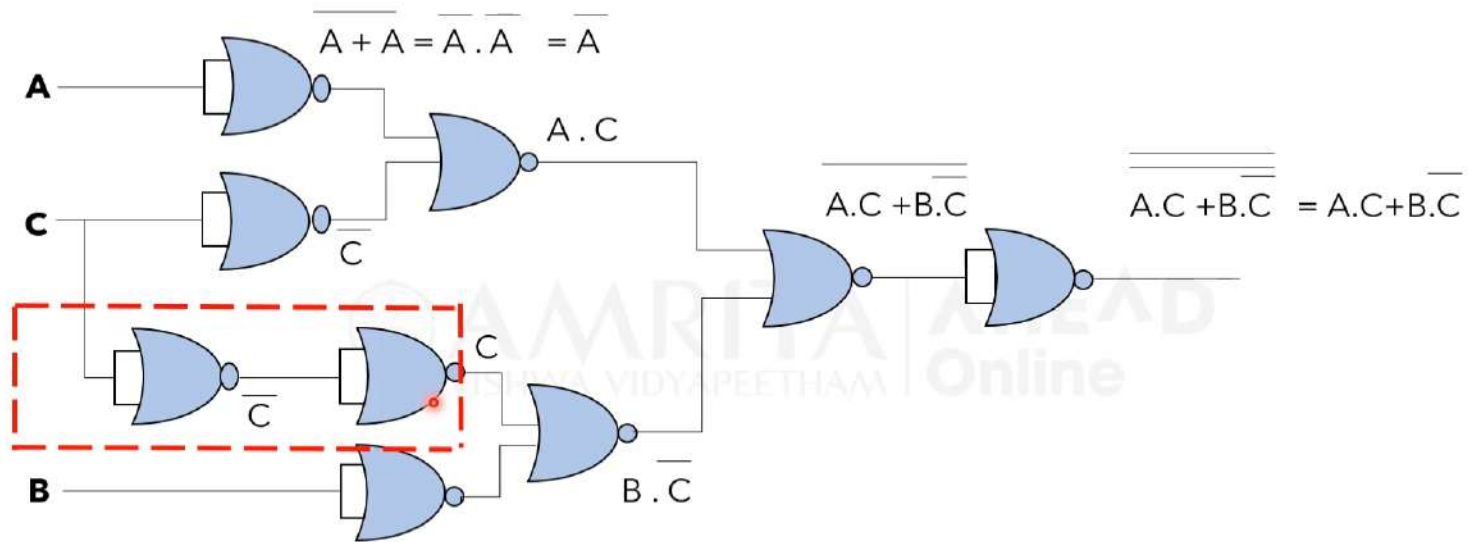

Summary

- Universal Logic gates






Canonical & Standard Forms

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

Representation of Boolean Function

- Standard form
- Canonical Form

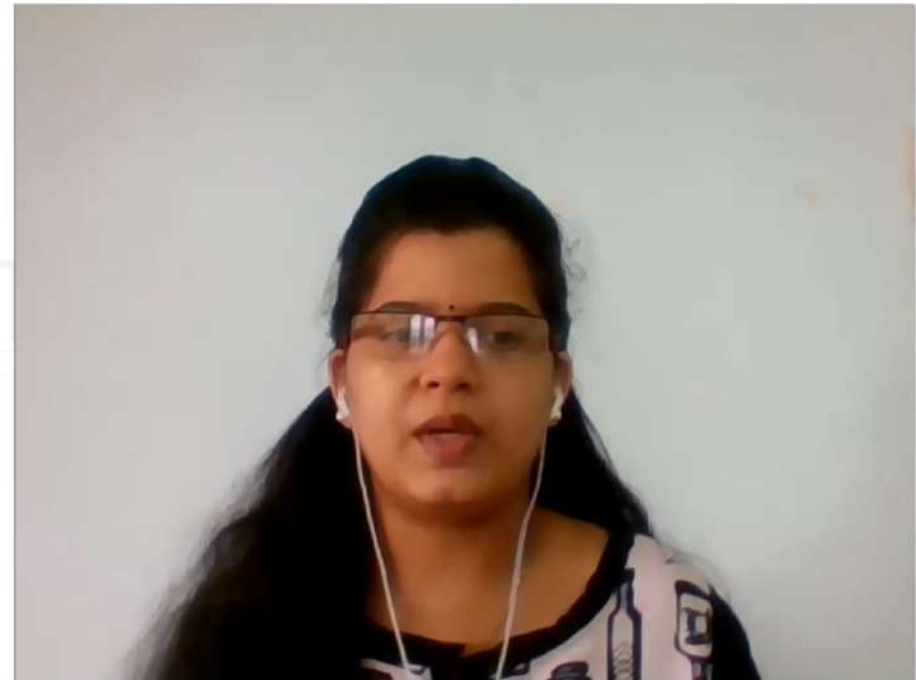

Introduction



- Boolean functions can be expressed in **canonical** and **standard forms**
 - In the Boolean expression binary variable will be either in normal form (x) or in its complement form (x').
- $F(A,B,C,D)$ is a function :
- **Product term** : Logical ANDed among the literals.
e.g., $AB, A'B, ABC'$
 - **Sum term** : Logical ORed among the literals.
e.g., $A+B, A'+B, A+B+C'$



Minterm : m_j

- **Minterm /Standard product** : Product term containing all the variables in normal or as complements.
e.g., $F(A,B,C) : ABC' , AB$
- For n- variable function have 2^n possible minterms.
- While obtaining minterm, each variable is complemented if the corresponding bit of binary number is 0 and uncomplemented if 1.

x	y	minterm	symbol
0	0	$x'y'$	m_0
0	1	$x'y$	m_1
1	0	xy'	m_2
1	1	xy	m_3

A minterm equals 1 at exactly one input combination and is equal to 0 otherwise.

e.g., $x'y' = 1$ only when $x = 0, y = 0$



Minterms with 2 binary variables x and y
2 variable - $2^2 = 4$ minterms
x is primed if $x=0$; x is unprimed if $x=1$

Minterms

- 3 variable function with $2^3 = 8$ possible minterms



A	B	C	minterm	symbol
0	0	0	$A'B'C'$	m_0
0	0	1	$A'B'C$	m_1
0	1	0	$A'BC'$	m_2
0	1	1	$A'BC$	m_3
1	0	0	$AB'C'$	m_4
1	0	1	$AB'C$	m_5
1	1	0	ABC'	m_6
1	1	1	ABC	m_7

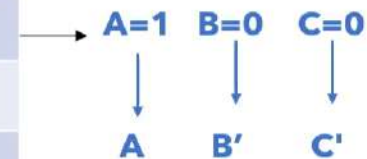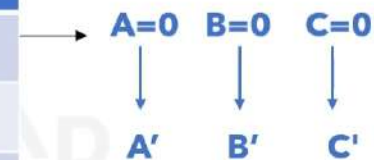

Expressing functions as Sum of Minterms



- Boolean function can be expressed algebraically from the truth table
 - Select the minterms that produces a 1 in the function.
 - Take OR of those selected minterms.

i.e., sum of all minterms

$$f = x'y'z + xy'z' + xyz$$

$$= m_1 + m_4 + m_7$$

$$= \Sigma(1,4,7)$$

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$x'y'z$ ←

$xy'z'$ ←

xyz ←

Expressing functions as Sum of Minterms




- Any function can be expressed by ORing all minterms (m_i) corresponding to input combinations (i) at which the function has a value of 1.
- Resulting expression is referred to as SUM of minterms and is expressed as $F = \Sigma(2, 4, 5, 7)$ where Σ indicates ORing of the indicated minterms.
- $F = \Sigma(2, 4, 5, 7) = (m_2 + m_4 + m_5 + m_7)$



Summary

- Canonical forms : Sum of Minterms

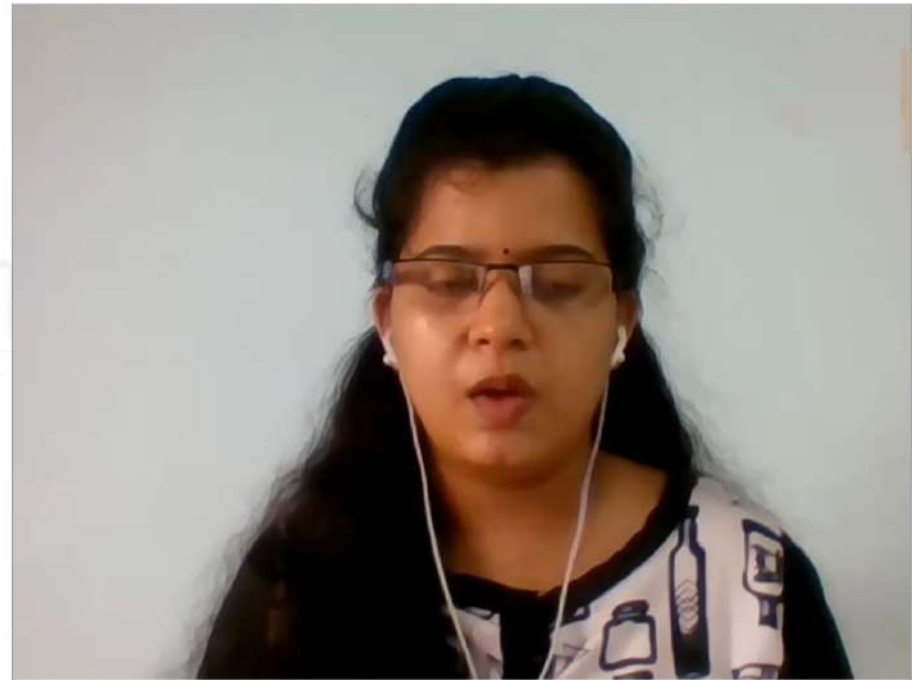



Canonical & Standard form-II

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- Canonical form and standard form using maxterms



Maxterm : M_j



- **Maxterm /Standard sums** : Sum term containing all the variables or their complements.
e.g., $F(A,B,C) : A+B+C'$, ~~$A \times C$~~
- For n - variables can have 2^n possible maxterms.
- For maxterm, each variable is primed if the corresponding bit of binary number is 1 and unprimed if 0

x	y	maxterm	symbol
0	0	$x+y$	M_0
0	1	$x+y'$	M_1
1	0	$x'+y$	M_2
1	1	$x'+y'$	M_3

A maxterm equals 0 at exactly one input combination and is equal to 1 otherwise.

e.g., $x+y' = 0$ only when $x = 0, y = 1$

Maxterms with 2 binary variables x and y
2 variable - $2^2 = 4$ maxterms
 x is primed if $x=1$; x is unprimed if $x=0$





Maxterms

- 3 variable function with $2^3 = 8$ possible maxterms



A	B	C	maxterm	symbol
0	0	0	$A+B+C$	M_0
0	0	1	$A+B+C'$	M_1
0	1	0	$A+B'+C$	M_2
0	1	1	$A+B'+C'$	M_3
1	0	0	$A'+B+C$	M_4
1	0	1	$A'+B+C'$	M_5
1	1	0	$A'+B'+C$	M_6
1	1	1	$A'+B'+C'$	M_7

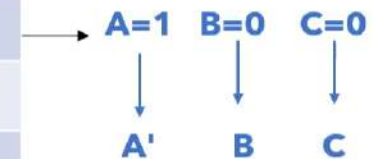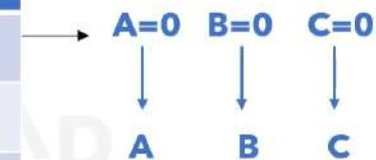

Expressing functions as Product of Maxterms



- Select maxterms that produces a 0 in the function
- Take AND of those selected maxterm

i.e., product of all maxterms

$$\begin{aligned}
 f &= (x+y+z)(x+y'+z)(x+y'+z')(x'+y+z')(x'+y'+z) \\
 &= M_0.M_2.M_3.M_5.M_6 \\
 &= \Pi(0, 2, 3, 5, 6)
 \end{aligned}$$

	x	y	z	f
$x+y+z \leftarrow$	0	0	0	0
	0	0	1	1
$x+y'+z \leftarrow$	0	1	0	0
$x+y'+z' \leftarrow$	0	1	1	0
	1	0	0	1
$x'+y+z' \leftarrow$	1	0	1	0
$x'+y'+z \leftarrow$	1	1	0	0
	1	1	1	1

Maxterm from Minterm



- Minterm and Maxterm are complement to each other.
- Complement of minterm = maxterm

Example : $F(x, y, z) = \Sigma (1, 4, 5, 6, 7)$

$F'(x, y, z) = \Sigma(0, 2, 3) = (m_0 + m_2 + m_3)$

x	y	z	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0



Karnaugh map

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- Systematic method of simplifying Boolean Expression - **Karnaugh map**



Introduction



- Pictorial representation of writing Boolean expression.
- The map method modified by Karnaugh is called **K-map** or **Karnaugh map**.
- Objective of K-map is the minimization of Boolean function with a simple procedure.
- K-map : Diagram made up of squares ; n-variable 2^n squares

Each square represents one minterm of the function

Visual diagram of a function in standard form(SOP or POS)



K-maps



- K-maps use 2-dimensional tables to simplify the Boolean expression.

A \ B	0	1
0	m_{00}	m_{01}
1	m_{10}	m_{11}

2-variable map

2 variable = $f(A,B)$

2^2 minterm = 4 cell map

A \ BC	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6

3-variable map

3-variable = $f(A,B,C)$

2^3 minterm = 8 cell map

AB \ CD	00	01	11	10
00	m_0	m_1	m_3	m_2
01	m_4	m_5	m_7	m_6
11	m_{12}	m_{13}	m_{15}	m_{14}
10	m_8	m_9	m_{11}	m_{10}

4-variable map

Adjacent cells differ by just one single bit

K- map Simplification



- First fill the appropriate cells with the value based on the output variable.
- Group the maximum number of 1's (SOP) and 0's (POS).
- Group need to be in power of 2 and done in decreasing order.
If 8 cell K-map, try grouping for 8 ($=2^3$), then for 4 ($=2^2$), next for 2 ($=2^1$) and last consider single bit.
- Later each group is expressed in terms of common input variable in the rows and column.



Grouping Rules



- Group the cells with largest number of consecutive 1's and no 0's .

correct

0	0	1	1
1	1	0	0

Incorrect

0	1	1	0
---	---	---	---

- Grouping must be done in decreasing order and the number of 1's in the group must be a power of 2.

incorrect

0	1	1	1
---	---	---	---

incorrect

1	1	1	1
1	1	1	1

correct

0	1	1	1
---	---	---	---

1	1	1	1
1	1	1	1

Grouping Rules



- Focus is on increasing the size of the group, so same elements can be repeated in multiple groups.

incorrect

1	1	1	1
0	1	1	0

correct

1	1	1	1
0	1	1	0

- Diagonal grouping is not permitted and elements around the edges can be grouped (circular property).

incorrect

1	0
0	1

correct

1	0	0	1
1	0	0	1

Summary

- Introduction to K-map with the simplification procedures





K-map simplification

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- K-map simplification examples





K-map Simplification



➤ $F(x,y) = x'y + xy' + xy$ (In SOP $x' = 0; x = 1$)


01 10 11

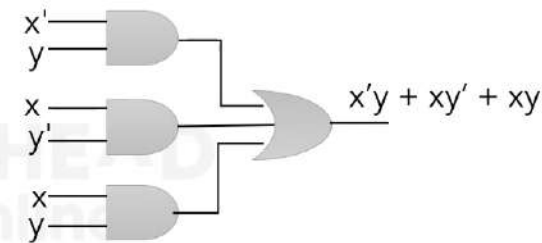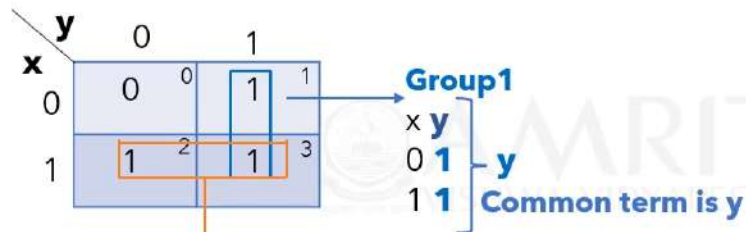With this expression we need **3 AND gates and 1 OR gate**



Simplified expression, $F(x, y) = x+y$

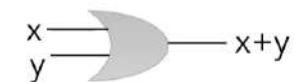Simplified expression need only 1 OR gate



Example(SOP)

➤ $Y(A,B,C,D) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$



AB \ CD	CD			
	00	01	11	10
00	1 ⁰	0 ¹	0 ³	1 ²
01	0 ⁴	1 ⁵	1 ⁷	0 ⁶
11	0 ¹²	1 ¹³	1 ¹⁵	0 ¹⁴
10	1 ⁸	0 ⁹	0 ¹¹	1 ¹⁰

$$Y = A'B'C'D' + A'B'CD' + A'BC'D + A'BCD + AB'C'D' + AB'CD' + ABC'D + ABCD$$

Group1

A B C D

0 1 0 1

0 1 1 1

1 1 0 1

1 1 1 1

} BD

Group2

A B C D

0 0 0 0

0 0 1 0

1 0 0 0

1 0 1 0

} B'D'

➤ Simplified expression $Y(A,B,C,D) = BD + B'D'$

Example(POS)



- $F(A,B,C,D) = \sum(0,1,2,5,8,9,10)$
 Given SOP but for simplification using POS group the 0's

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1

Group1

AB	CD
00	11
01	11
11	11
10	11

$C' + D'$

Group2

AB	CD
11	00
11	01
11	11
11	10

$A' + B'$

Group3

A	B	C	D
0	1	0	0
1	1	0	0
0	1	1	0
1	1	1	0

$B' + D$

- Simplified expression $F(A,B,C,D) = (C'+D')(A'+B')(B'+D)$

Example(Don't care)



- Functions can have unspecified output for some input combination, we don't care the value of those unspecified terms.
- $F(A,B,C,D) = \sum (1,3,5,7,9) + d(6,12,13)$

AB \ CD	CD			
	00	01	11	10
00	0	1	1	0
01	0	1	1	X
11	X	X	0	0
10	0	1	0	0

Group1

A B C D

0 0 0 1

0 0 1 1

0 1 0 1

0 1 1 1

A'D

Group2

A B C D

0 0 0 1

0 1 0 1

1 1 0 1

1 0 0 1

C'D

$$F(A,B,C,D) = A'D + C'D$$

Without don't care
 $F(A,B,C,D) = A'D + B'C'D$



Summary

- Explained how to perform K-map simplification with examples

