



Sequential circuits

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- Introduction to sequential circuits.




Sequential circuits



- Combinational circuits = no memory (inputs — outputs)
- Sequential circuit output depends not only on the present value of the input but also on previous value of the input signal.
- Sequential circuits = Combinational circuits + memory elements.
- Sequential circuit uses a memory element like flip-flops as feedback circuit to store past values.



Sequential circuits

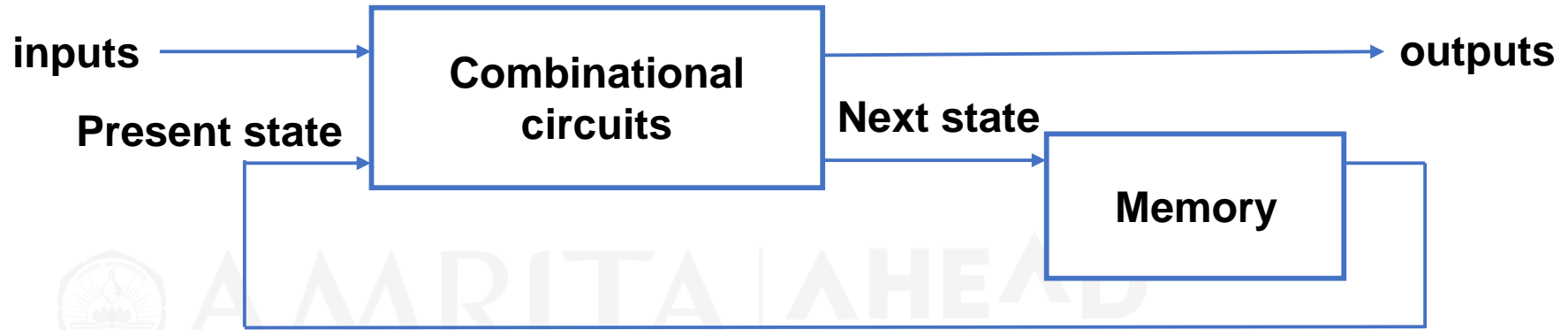

Block diagram of sequential circuit


- Memory : device capable of storing binary information i.e., state.
- (inputs , present state) \longrightarrow (outputs , next state)



Clock Signal in Sequential circuit



 
- A clock is a signal which oscillate between logic level 0 and logic level 1 repeatedly.
- Sequential circuit retains its state till the next clock edge occurs



Sequential circuits



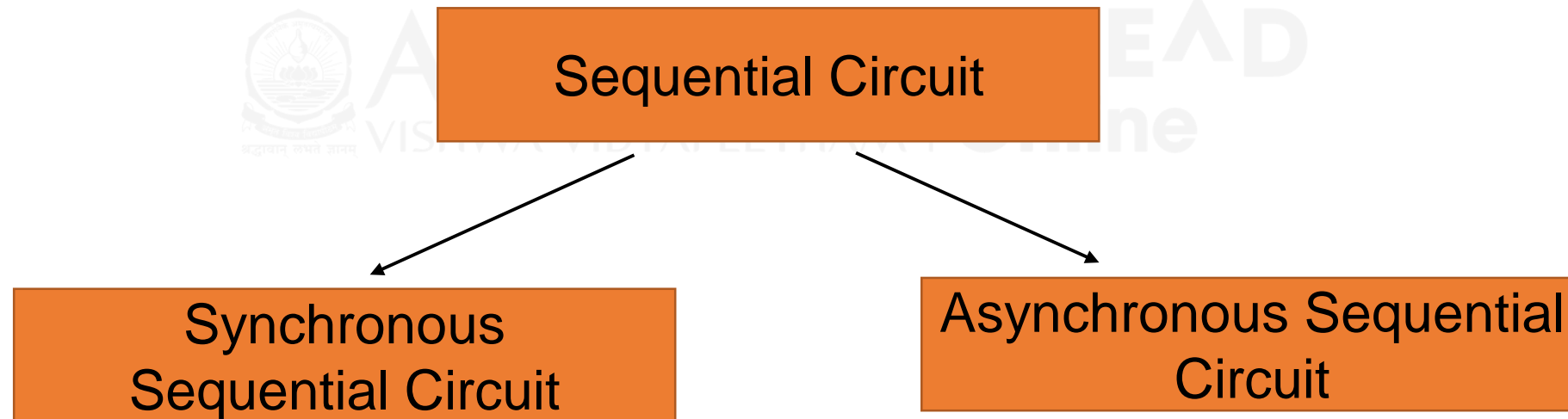- Two types based on the timings of signal




Synchronous Sequential circuit



- Synchronization is achieved by a timing signal called master-clock generator which generates a periodic clock pulses.
- SS circuits using clock pulses in the input of memory elements are called clocked sequential circuits.
- Clock signal is used to control the exact time at which any output can change its state.
- Memory in clocked sequential circuits are designed using **flip flops**.



Synchronous Sequential circuit

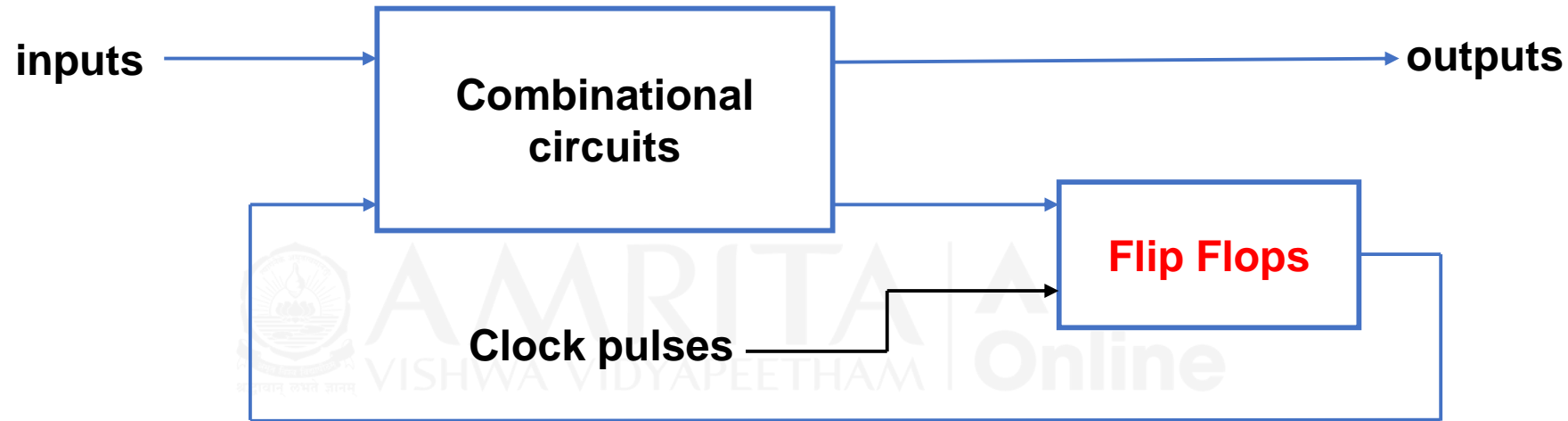


Block diagram of Synchronous sequential circuit

- Flip flops receive inputs from combinational circuits and from clock signal with pulse that occur at fixed interval of time.

Asynchronous Sequential circuits



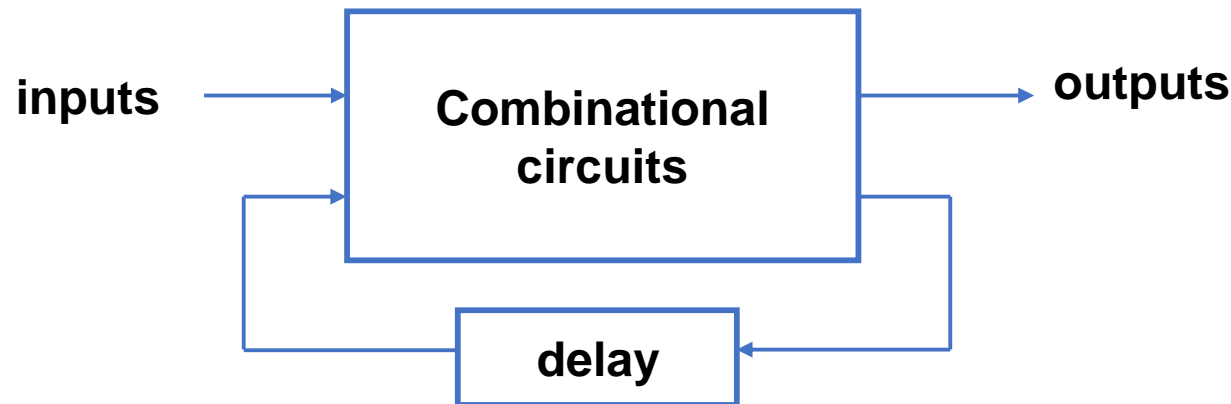- System behavior depends on the order in which its input signals change and can occur at any instant of time.
- Do not use clock pulses, so change of state occur at any time.
- Memory elements used are latch or time delay elements.



Summary

- Explained about sequential circuits



Reference

- M Morris Mano - Computer System Architecture - PHI - Third Edition
- Gideon Langholz, Abraha& Joe L Mott - Digital Logic Design - World Scientific Publishing Co Ltd
- Thomas C Bartee - Digital Computer Fundamentals - Tata Mc Graw Hill - Sixth Edition



Flip Flops

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- Introduction to basic building blocks of memory in digital systems : **FLIP-FLOPS**



Introduction



- **Flip-flops** are the building blocks of most sequential circuits.
- Flip-flops used as memory elements can store one bit of information.
- Clocked flip-flop serve as the memory element in synchronous sequential circuits.
- Unclocked flip-flops (latches) act as the memory element in asynchronous sequential circuits.
- Output in sequential circuit is from combinational circuit or flip-flop or both.



Basic Flip-flop circuits




- Flip-flops can be constructed using two NAND gates or two NOR gates.
- Cross-coupled connection from the output of one gate to the input of the other is the feedback path.
- 4 types of flip-flops : SR flip-flop, JK flip-flop, D flip-flop, T flip-flop.
- Application of flip-flop : Counters
 - Shift Register
 - Storage Register



SR latch with NAND gate



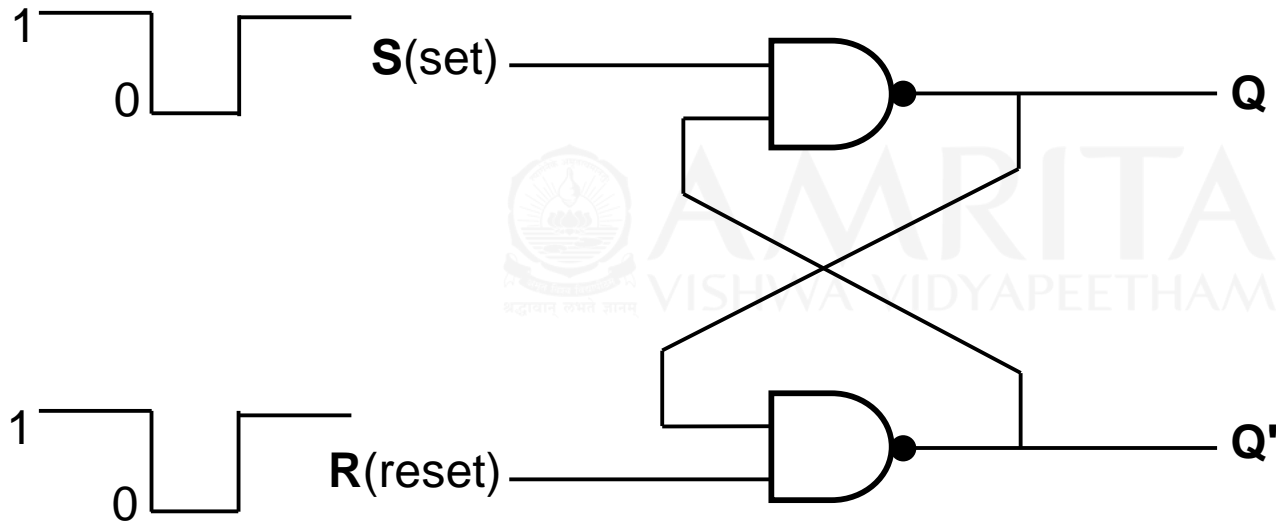- Most basic sequential logic circuit with inputs “**SET**” (output = 1) and “**RESET**”(output = 0).



Logic diagram


Truth table

S	R	Q	Q'	
1	0	0	1	reset
1	1	0	1	No change
0	1	1	0	set
1	1	1	0	No change
0	0	-	-	undefined

For NAND gate, if any input is 0, output is 1
 $R = S = 1$;keep previous state



SR Latch with NOR gate

 

Logic diagram

Truth table

S	R	Q	Q'	
1	0	1	0	set
0	0	1	0	No change
0	1	0	1	reset
0	0	0	1	No change
1	1	-	-	undefined

For NOR gate, if any input is 1, output is 0
 $R = S = 0$; keep previous state

Summary

- Explained about fundamentals of flip-flops



Reference

- M Morris Mano - Computer System Architecture - PHI - Third Edition
- Gideon Langholz, Abraha& Joe L Mott - Digital Logic Design - World Scientific Publishing Co Ltd
- Thomas C Bartee - Digital Computer Fundamentals - Tata Mc Graw Hill - Sixth Edition



Flip Flops-II

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective


- Introduction to clocked flip-flops



Clocked Flip-flops



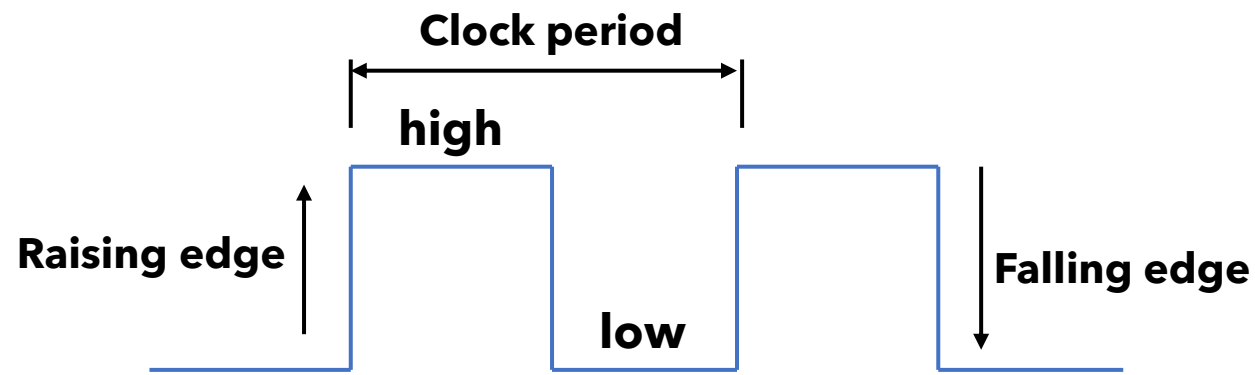
- Operation of basic flip-flop can be modified by an additional control input which determine the change of state in circuit.
- Basic flip-flop circuits with additional NAND gates.
- Clock Pulse input act as the other inputs.



RS Flip-flop



 - Basic flip-flop circuit with 2 additional NAND gates.



Logic diagram

Q	S	R	Q_{t+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	Indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	Indeterminate

Characteristic table



RS flip-flop



- Characteristic equation

$$Q_{t+1} = S + R'Q$$


$$SR = 0$$

Next state = (present state, inputs)

SR \ Q	00	01	11	10
0			X	1
1	1		X	1

- Given present state and the inputs S, R of a single pulse in the input go to the next state Q_{t+1} in flip-flop.



Graphic symbol

 

D Flip-flop



 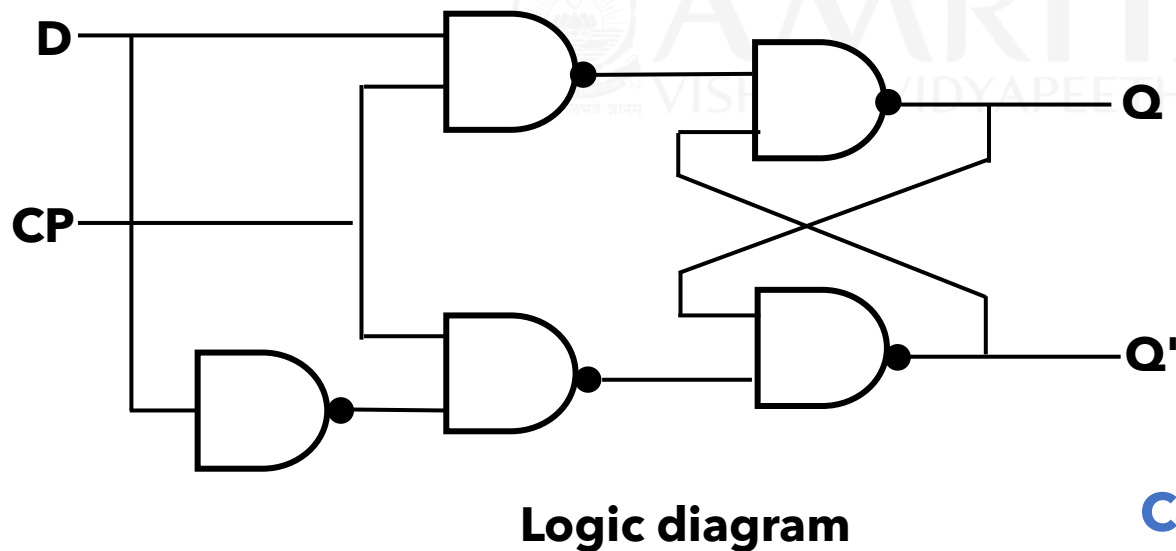- To eliminate the intermediate state in RS flip-flop by never having value 1 to the inputs at the same time.
- Modification of RS flip-flop



Q	D	Q _{t+1}	
0	0	0	
0	1	1	
1	0	0	reset
1	1	1	set


Q \ D	0	1
0		1
1		1

Characteristic equation, $Q_{t+1} = D$


JK Flip-flop



 - Refinement of RS flip-flop with definition for the intermediate state is JK type.



Q	J	K	Q _{t+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


$$Q_{t+1} = JQ' + K'Q$$

- If J and K are both high at the clock edge, output will toggle from one state to the other

T flip-flop



 - T means the ability of flip-flop to “toggle” or complement its state.
- Flip-flop complements its output when the clock pulse occurs while input is 1, regardless of present state.



Q	T	Q _{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

$$\begin{aligned}Q_{t+1} &= TQ' + T'Q \\ &= T \oplus Q\end{aligned}$$



Excitation Table



- Characteristic table specifies the next state of flip-flop given inputs and present state.
- Excitation table : For a particular transition to take place what should be the inputs.(if Q is 0 and to get Q' as 1 what should be the inputs)

Q	Q_{t+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

RS flip-flop

Q	Q_{t+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK flip-flop

Q	Q_{t+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

D flip-flop

Q	Q_{t+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

T flip-flop



Summary

- Basics of RS, D, T and JK flip-flops



Reference

- M Morris Mano - Computer System Architecture - PHI - Third Edition
- Gideon Langholz, Abraha& Joe L Mott - Digital Logic Design - World Scientific Publishing Co Ltd
- Thomas C Bartee - Digital Computer Fundamentals - Tata Mc Graw Hill - Sixth Edition



Registers

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- Fundamentals about Registers



Introduction




- One flip-flop can store one bit of information.
- A group of flip-flops which can store multiple bits of information is called a **register**.
- Register is a device used to store information.
- **n-bit register** has a group of n flip-flops capable of storing n-bit binary information's .
- To store 16-bit data need a set of 16 flip-flops



Registers



 - Simplest register consist of only flip-flops without any external gates.



- Clock pulse enables all flip-flops, so the information at four inputs can be transferred into the 4-bit register.

Shift Registers



- Binary data in a register can be moved within the register from one flip-flop to another.
- **Shift register** : Sequential logic circuit capable of storing and transferring of binary data.
- It can shift its binary data either to the right or to the left.
- Simplest possible shift register is the one with flip-flops only.



Shift register Operations



- There are four mode of operations of a shift register.
 - Serial Input Serial Output (SISO)

Only 3 connections: Serial input (SI) to left flip-flop, serial output (SO) from right flip-flop and sequencing clock signal.

Operation:


Initially $Q_3Q_2Q_1Q_0 = 0000$

IN = $D_3 = 1$; Apply clock; FF3 set; $Q_3 = 1$

IN = 1; FF2 set; $Q_3Q_2 = 11$

IN = 0; FF1 set; $Q_3Q_2Q_1 = 011$

IN = 1; FF0 SET; $Q_3Q_2Q_1Q_0 = 1011$

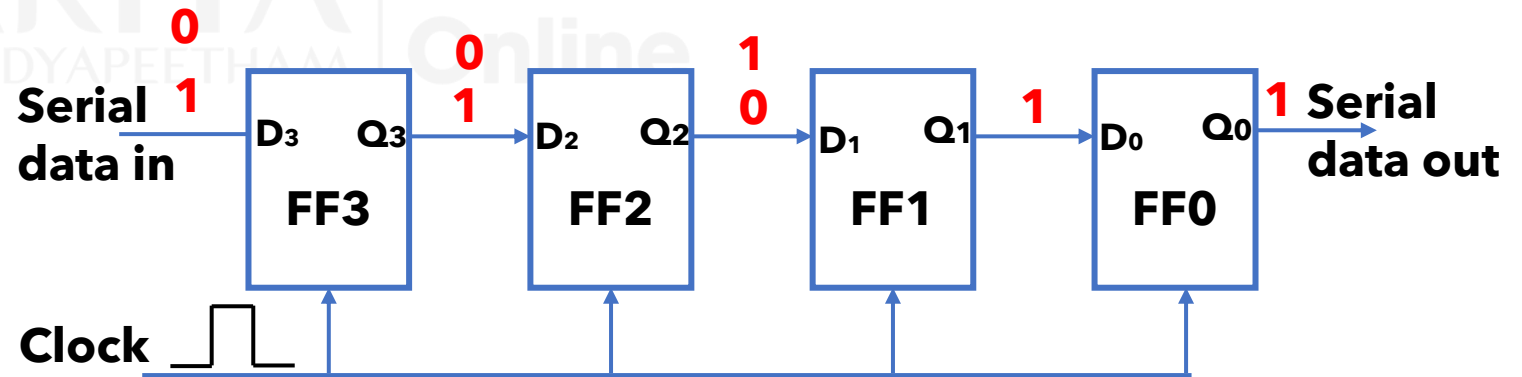

Act as temporary storage or time delay device



Mode of Operations




➤ Serial Input Parallel Output (SIPO)

- Data entered serially and taken out in parallel fashion.
- Data loaded bit by bit. Output disabled while data is loading.
- Once data loading completed, flip-flops contain the required data , outputs are enabled thus data is available at the same time.

4-bit word need clock cycles

Speed : SISO = SIPO

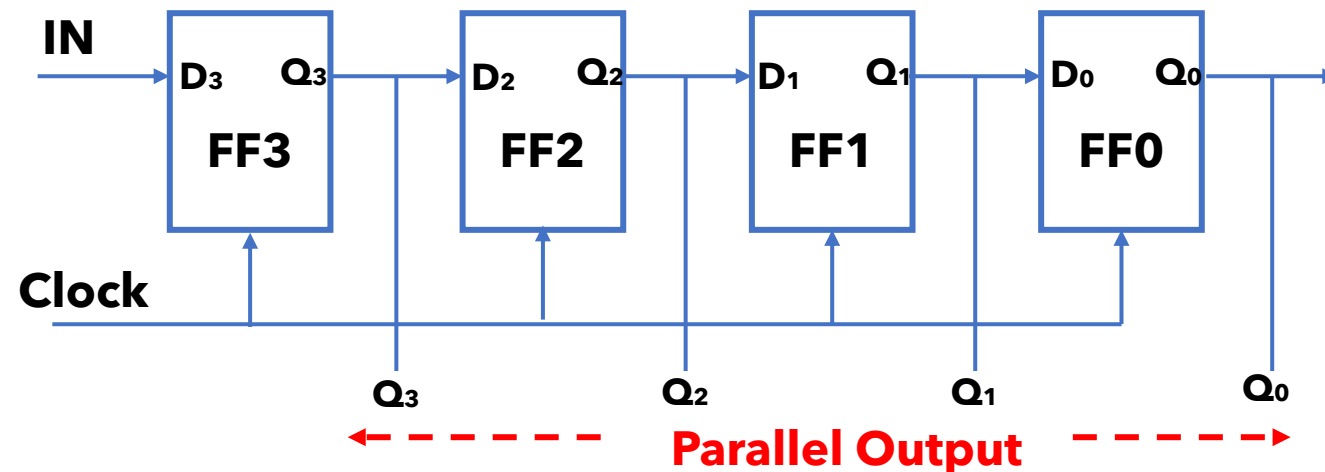

Mode of Operations



➤ Parallel Input Serial Output(PISO)

- Opposite of SIPO
- Data is loaded into the register in parallel format i.e., all data bits enter their input simultaneously.
- Data is outputted one bit in each clock cycle in a serial format.

➤ Parallel Input Parallel Output(PIPO)

- Data is loaded and unloaded in parallel format.
- One clock pulse loads and unloads the register.
- Also act as temporary storage or delay device as SISO.



Universal Shift Register



- Shift register capable of shifting in one direction is called unidirectional shift register.
- Shift register shifting in both direction are bi-directional shift register.
- Universal shift register : Shift data in both direction as well as load it parallelly.
- Operations: Parallel loading, Left shifting, Right shifting



Application of Registers



- Temporary data storage
- Data transfer
- Data manipulation
- As counters



Summary

- Explained about Registers



Reference


- M Morris Mano - Computer System Architecture - PHI - Third Edition
- Gideon Langholz, Abraha& Joe L Mott - Digital Logic Design - World Scientific Publishing Co Ltd
- Thomas C Bartee - Digital Computer Fundamentals - Tata Mc Graw Hill - Sixth Edition



Counters

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham


Objective

 

Introduction



 
- **Counter** is a sequential digital device used for counting(up or down).
- It is a group of flip-flops which outputs sequence of states on applying clock signal as input.
- **n-bit binary counter** consist of n flip-flops and count in binary from 0 to $2^n - 1$.



Design of 3-bit Binary Counter



↓
 0 to $2^3 - 1$

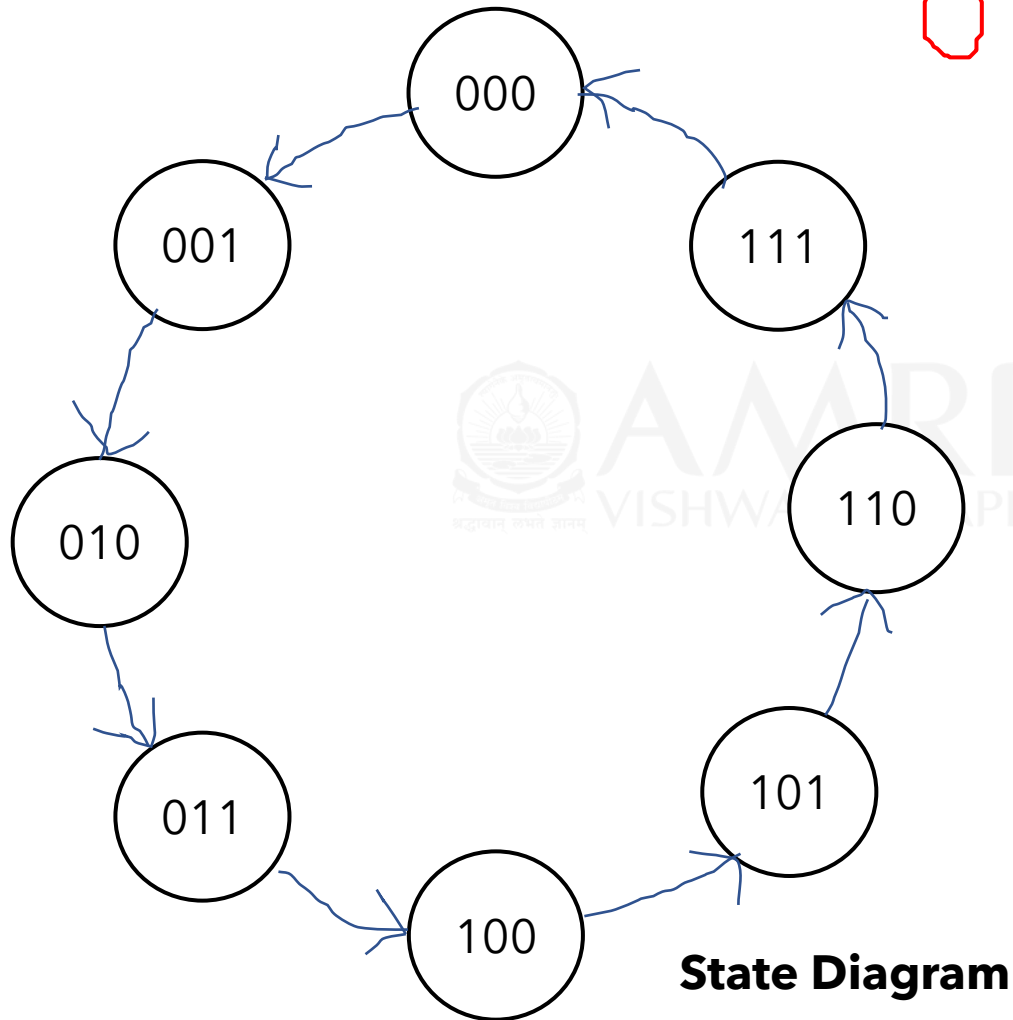


	P.State	N.State	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

Excitation Table

Asynchronous Counter (Ripple Counter)



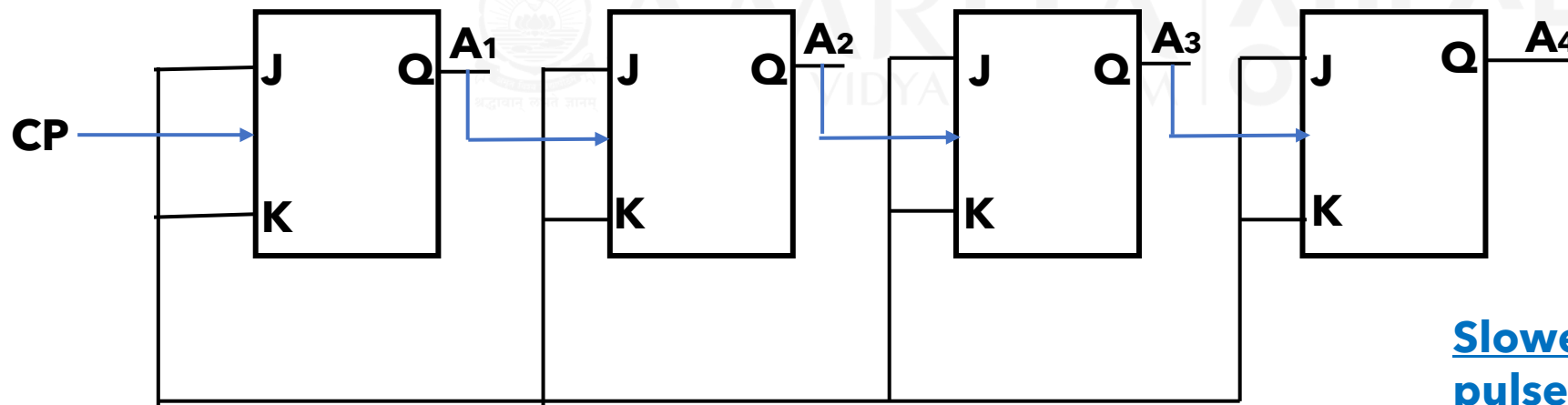- The flip-flop output transition serves as the input for triggering other flip-flops. The input pulse is applied only to the first flip-flop.



Slower - delay in transmission of pulse from flip-flop to flip-flop

4-bit binary ripple counter



Synchronous counter



- Clock pulses are applied to the CP inputs of all flip-flops so the delay problem in ripple counter get solved.
- Common clock pulse triggers all the flip-flops simultaneously unlike ripple counter.
- Synchronous counters have a regular pattern and can be constructed by complementing the flip-flops and gates.
- Design is complex when compared to asynchronous counter.



Difference



Synchronous Counter	Asynchronous Counter
All flip-flops are triggered with same clock	Different clock is applied to different flip-flops
Faster	Slower
Design is complex	Design is comparatively easy
Any flip-flop can be used	All flip-flops are toggle flip-flops
Expensive	Less costly



Application of Counter



- Frequency counter
- Digital clocks
- Analog to digital converter
- Time measurements



Summary

- Explained about counters, different types of counters along with its application



Reference

- M Morris Mano - Computer System Architecture - PHI - Third Edition
- Gideon Langholz, Abraha& Joe L Mott - Digital Logic Design - World Scientific Publishing Co Ltd
- Thomas C Bartee - Digital Computer Fundamentals - Tata Mc Graw Hill - Sixth Edition

