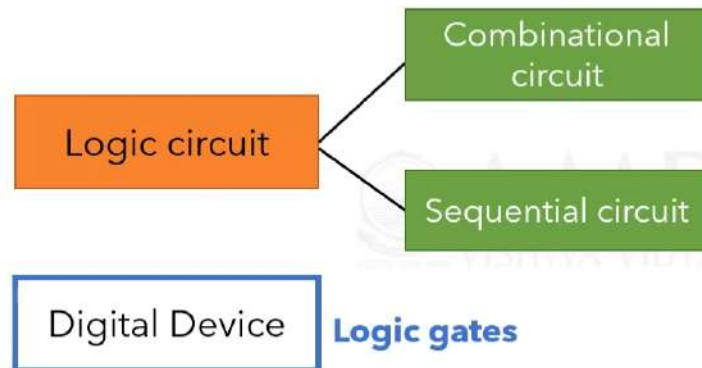




Combinational circuits

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective



Introduction



- Logic circuits for digital systems can be combinational or sequential.
- Combinational circuits consist of input variables, logic gates and output variables.
- Outputs are determined from the present input states not on previous states.



Block diagram of combinational circuit

n inputs - 2^n input combinations

For each input combination, only one possible output.



Combinational Circuit Design



- The problem is stated
- The input and output variables are assigned letter symbols
- Truth table is derived
- The simplified Boolean function for each output are obtained
- The logic diagram is drawn.



Combinational Circuits

- Adders
 - Subtractors
 - Comparators
 - Decoders
 - Encoders
 - Multiplexers
 - Demultiplexers
- Arithmetic and logic functions**
- Data Transmission**



Adder



- Basic arithmetic operation in digital computer is binary addition.
- The combinational circuit which performs the addition of binary digits are called **adder**.
- **Half-adder** : Circuit performing the addition of 2 bits. $\begin{array}{r} 1/0 \\ 1/0 \end{array}$
- **Full-adder** : Circuit performing the addition of 3 bits. — — —
- Binary addition rules : $0+0=0$; $0+1=1$; $1+0=1$; $1+1=0$ with carry 1




Half Adder




- 2 binary inputs augend and addend bits with 2 binary output called **sum** and **carry**.

inputs		outputs	
A	B	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Truth table

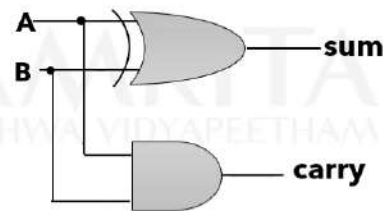

Logic diagram

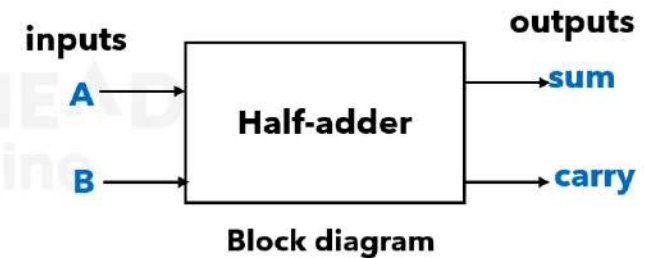

Block diagram

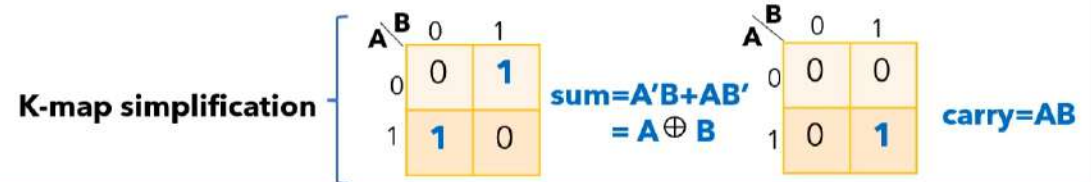

Full Adder



- Arithmetic sum of 3 input bits where third bit is previous carry bit.



A \ BC				
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$\text{sum} = A'B'C + A'BC' + AB'C' + ABC$$

A \ BC				
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$\text{carry} = AC + BC + AB$$

inputs			outputs	
A	B	C _{in}	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1




Full Adder



- A full adder can be implemented with 2 half adders and 1 OR gate

- sum** = $A'B'C + A'BC' + AB'C' + ABC$
 $= C \oplus (A \oplus B)$

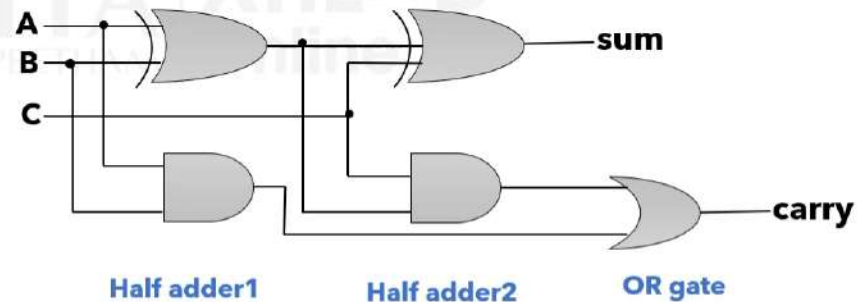- carry** = $AB + BC + AC$
 $= AB + C(A \oplus B)$



Logic circuit of full adder

Summary

- Discussed basic arithmetic combinational circuits called adders






Subtractors & Comparator

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

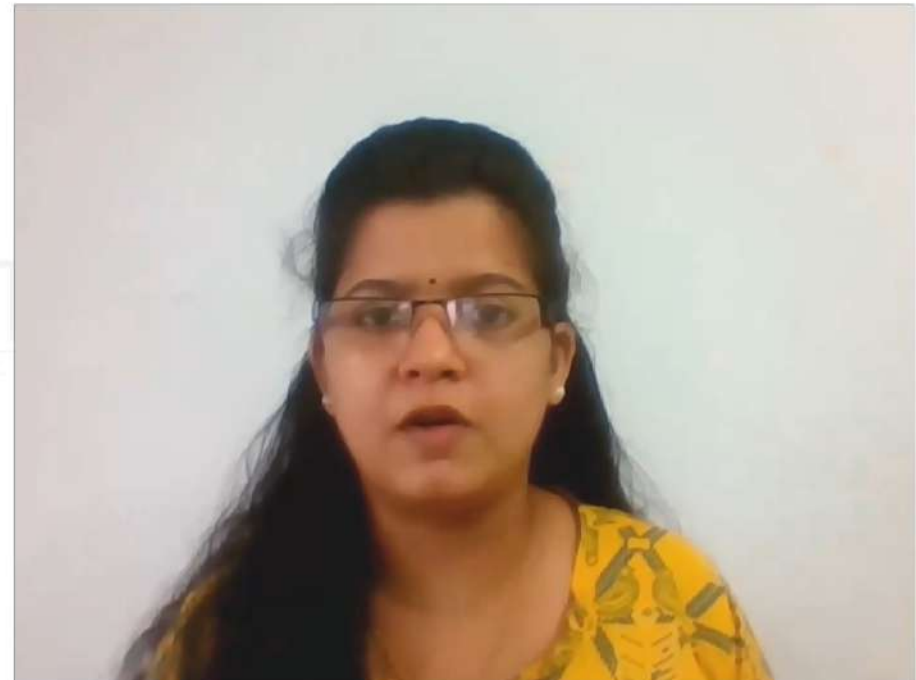- Combinational circuits
 - Subtractors
 - Comparators



Subtractors



- Logic circuit to **subtract** binary numbers.
- Difference and borrow are the outputs.
- **Half subtractors** : circuit for subtracting 2 bits.
- **Full subtractors** : circuit for subtracting 3 bits.
- Binary subtractor rules : $0-0=0$; $0-1=1$ with borrow 1 ; $1-0=1$; $1-1=0$



Half subtractors


1/0 1/0



- 2 binary input bits with 2 binary output called difference and borrow.

inputs		outputs	
A	B	diff	borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Truth table

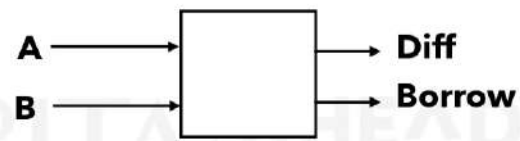


$$\text{Diff} = A'B + AB'$$
$$= A \oplus B$$

$$\text{Borrow} = A'B$$

	B	0	1
A	0		1
	1	1	

	B	0	1
A	0		1
	1		

K-map simplification

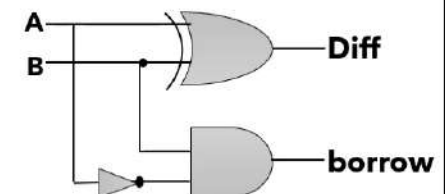

Logic diagram

Full subtractors



- 3 inputs minuend, subtrahend, previous borrow with 2 outputs difference and borrow.


inputs			outputs	
x	y	z	diff	borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

x \ yz	00	01	11	10
0		1		1
1	1		1	

$$\text{Diff} = x'y'z + x'yz' + xy'z' + xyz$$

x \ yz	00	01	11	10
0		1	1	1
1			1	


$$\text{Borrow} = x'z + yz + x'y$$

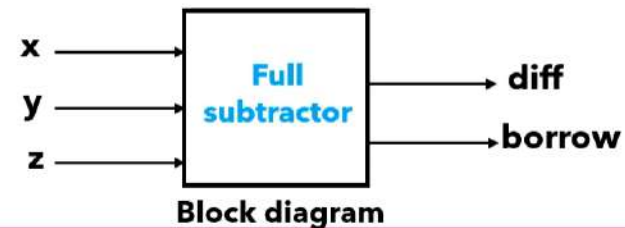

Magnitude Comparator



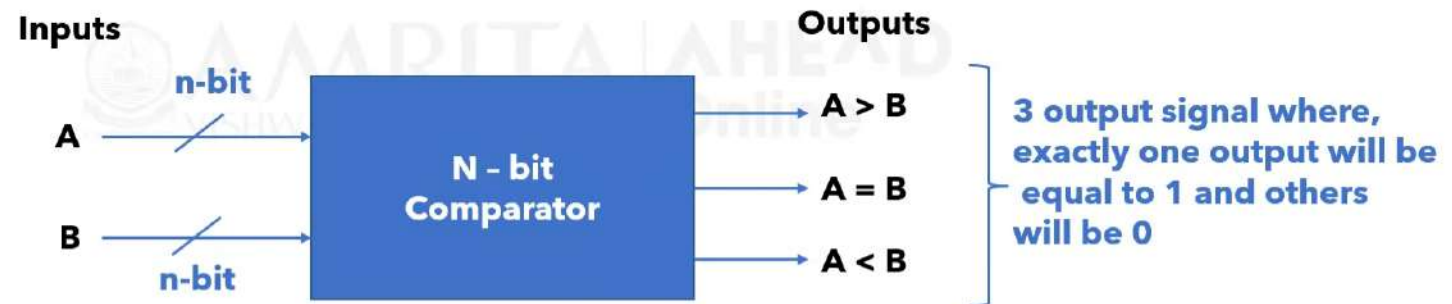- A combinational circuit that compares two numbers A & B to determine whether: $A > B$ or $A = B$ or $A < B$



1-bit Comparator





- To compare two single bit number

A	B	A>B	A=B	A<B
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0


$A > B : AB'$ $A < B : A'B$

$A = B : A'B' + AB$

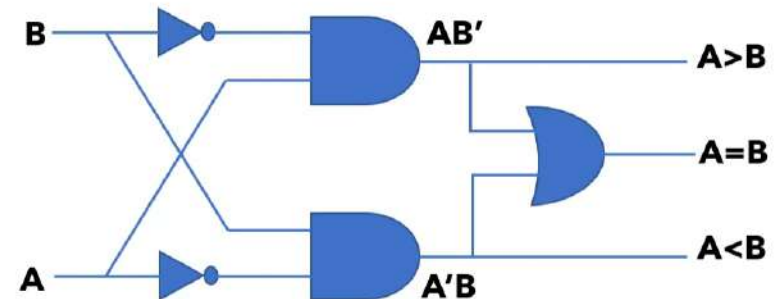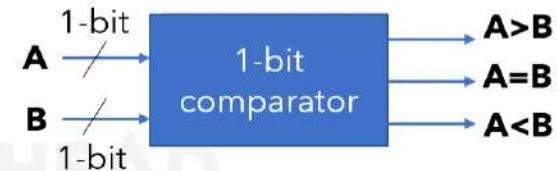

Summary

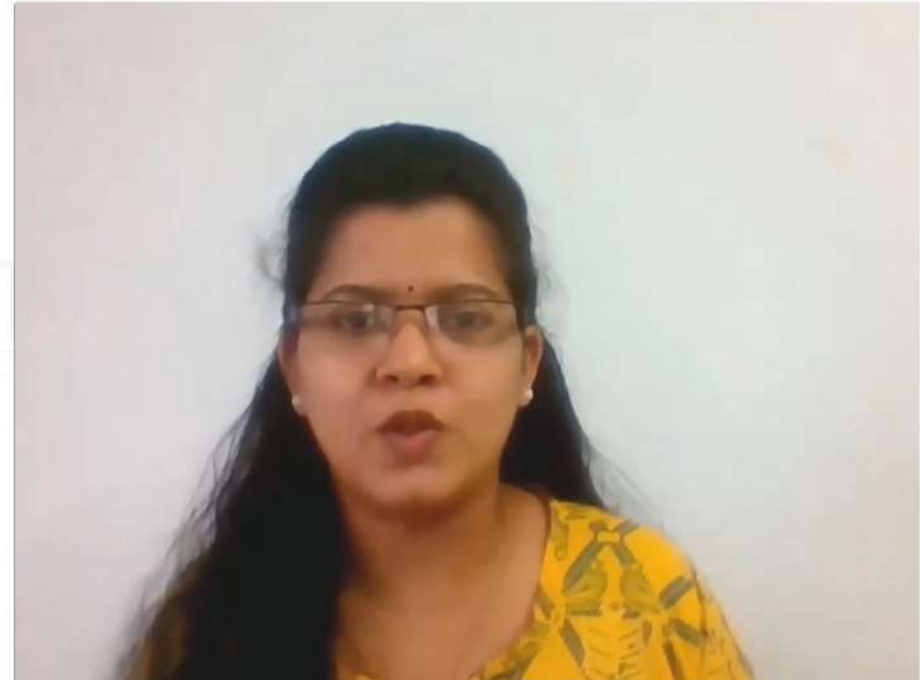- Explained combinational circuits called subtractors and comparators





Parallel adders & subtractors

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective


- Combinational circuits :
Parallel adders and
subtractors



Binary Parallel Adder



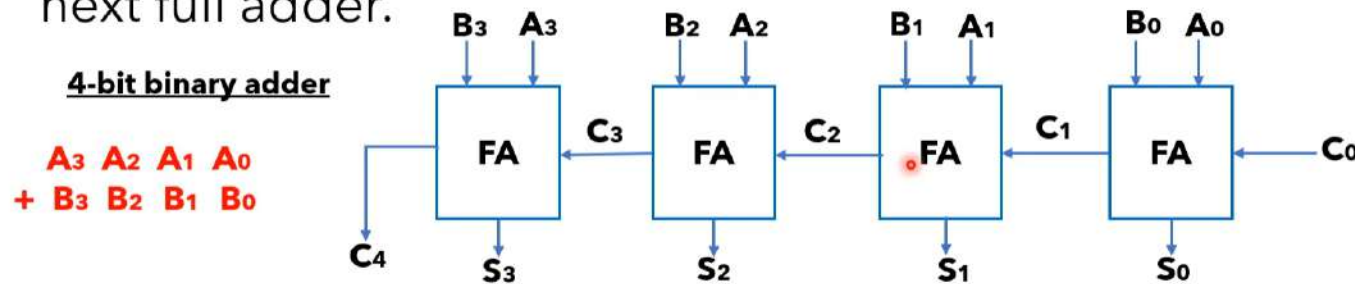- Digital circuit which perform the arithmetic addition of 2 binary numbers in parallel by cascading full adders.
- To add two n-bit binary numbers we need **n-bit binary adder**.
- Connect the carry output of each full adder to the carry input of the next full adder.




4-bit binary adder example



➤ Addition of decimal numbers 11 and 3


Augend	11	Binary addition	MSB	LSB
Addend	3	Augend(Ai)	1	0
		Addend(Bi)	0	1
sum	14	Carry (Ci)	0	1
Carry	0	Sum(Si)	1	1
		Carry out	0	

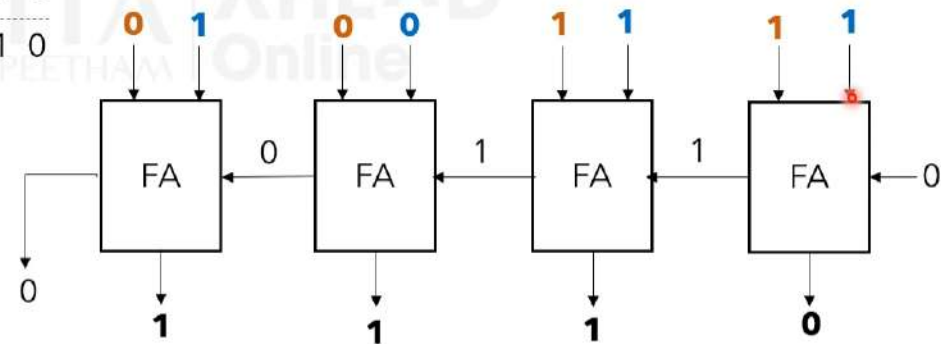

Binary Parallel Subtractor



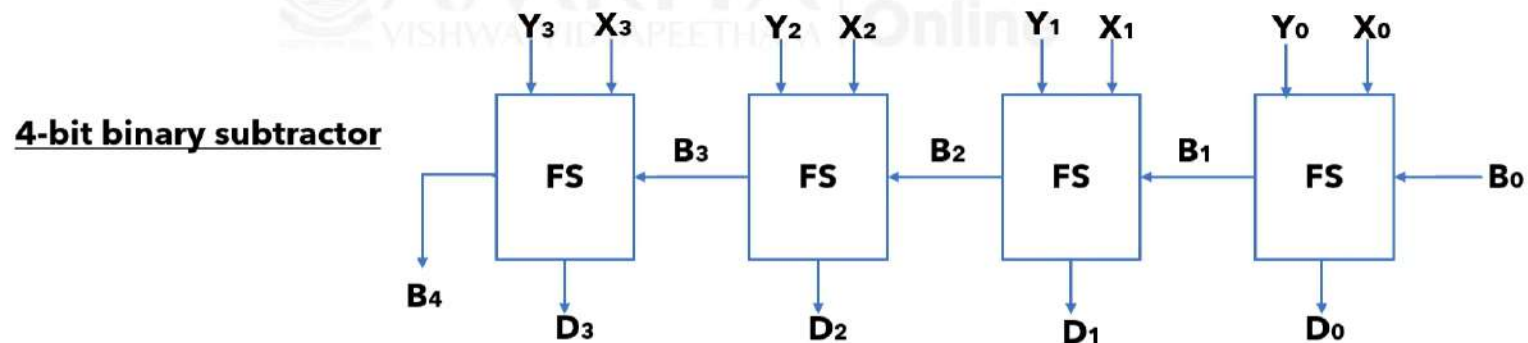- Digital circuit which perform the arithmetic subtraction of 2 binary numbers in parallel by cascading full subtractors.
- Binary adder can also be used to perform binary subtraction.



Summary

- Explained how to perform n-bit binary numbers arithmetic operations using Parallel adders and subtractors





Data Transmission circuits

Ms. Prathibha Prakash
Department of Computer Science
Amrita Vishwa Vidyapeetham

Objective

- Data transmission circuits
 - Decoders
 - Encoders
 - Multiplexers
 - Demultiplexers



Decoders




- n-bit binary number can represent maximum 2^n distinct elements of coded information.
e.g., 3-bit : 8 elements (000 - 111)
- **Decoder** is a combinational circuit with n input lines and maximum of 2^n output lines.
- One of the output will be high based on the combination of input lines.
- Translate coded information from one format to another



Decoders



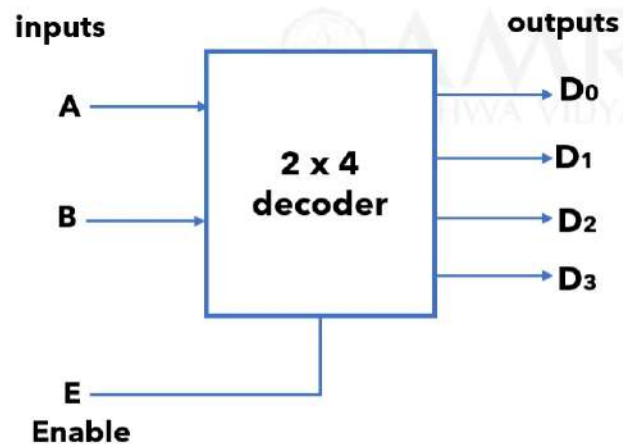- Decoder represented as $n \times 2^n$ provides the 2^n minterms of n input variables.




Enable	inputs		outputs			
E	A	B	D ₀	D ₁	D ₂	D ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Out of 4 outputs, only one input combination is high when enabled

Encoders



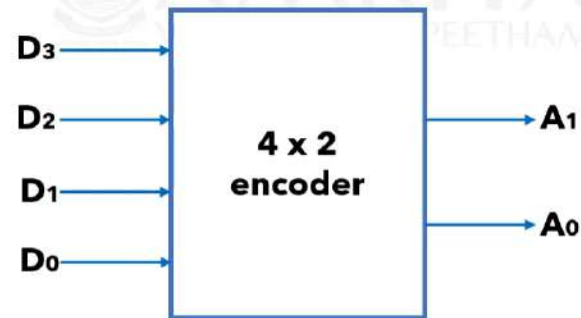- Encoders are combinational circuit that performs the reverse operation of decoders.
- It has 2^n input lines and n output lines.



inputs				outputs	
D_3	D_2	D_1	D_0	A_1	A_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

$$A_0 = D_3 + D_1$$

$$A_1 = D_2 + D_3$$



Priority Encoder



- An encoder circuit with priority function.
- If two or more inputs are equal to 1 at the same time, the input with **highest priority** will be considered.

- After K-map simplification

$$A_1 = D_2 + D_3$$

$$A_0 = D_3 + D_1 D_2'$$


$$v = D_0 + D_1 + D_2 + D_3$$

inputs				outputs		
D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	v
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

Multiplexers



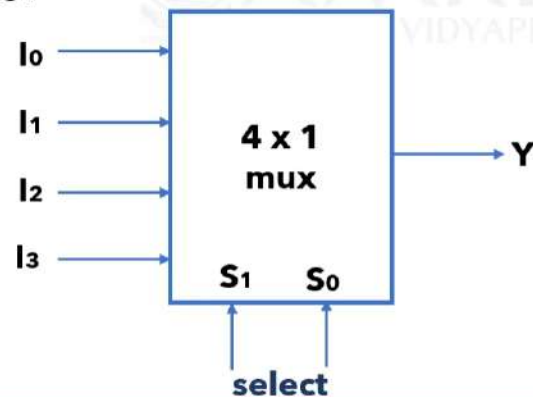- Combinational circuit with **2^n input lines, n selection lines** whose bit combination determine input to be selected and a **single output line**.
- Also called data selector, since it selects one of many inputs and outputs.




S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3



De-multiplexers



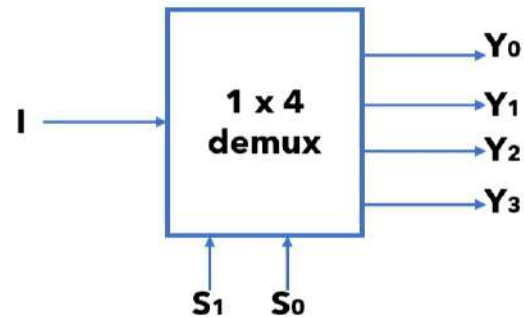- Combinational circuit that performs the reverse operation of multiplexer.
- It has one input line , n select lines to choose one output out of 2^n possible output lines.



S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Summary

- Discussed data transmission combinational circuits

